

CO502 - Advanced Computer Architecture
Part 02 (Hardware Units)
Group 04

Group Members

E/18/077 - Nipun Dharmarathne
E/18/397 - Shamod Wijerathne
E/18/402 - Chathura Wimalasiri

Instruction types and their encoding formats

There are 6 types of instructions in RISC-V architecture:

1. R-type (register-type) instructions: These instructions operate on registers and have three register operands. Examples include ADD, SUB, AND, OR, XOR, SLL, SRL, and SRA.

 


Figure 01: R-type instruction encoding format

Here, the funct7, funct3, and opcode fields identify the specific operation, while the rs1, rs2, and rd fields specify the source and destination registers.

The instruction performs the operation specified by funct3 on the values stored in the two source registers rs1 and rs2. The result of the operation is stored in the destination register rd. The specific operation performed by the instruction depends on the function code funct3.

| | | | | | | |
|---------|-----|-----|-----|----|---------|------|
| 0000000 | rs2 | rs1 | 000 | rd | 0110011 | ADD |
| 0100000 | rs2 | rs1 | 000 | rd | 0110011 | SUB |
| 0000000 | rs2 | rs1 | 001 | rd | 0110011 | SLL |
| 0000000 | rs2 | rs1 | 010 | rd | 0110011 | SLT |
| 0000000 | rs2 | rs1 | 011 | rd | 0110011 | SLTU |
| 0000000 | rs2 | rs1 | 100 | rd | 0110011 | XOR |
| 0000000 | rs2 | rs1 | 101 | rd | 0110011 | SRL |
| 0100000 | rs2 | rs1 | 101 | rd | 0110011 | SRA |
| 0000000 | rs2 | rs1 | 110 | rd | 0110011 | OR |
| 0000000 | rs2 | rs1 | 111 | rd | 0110011 | AND |

| | | | | | | |
|---------|-----|-----|-----|----|---------|--------|
| 0000001 | rs2 | rs1 | 000 | rd | 0110011 | MUL |
| 0000001 | rs2 | rs1 | 001 | rd | 0110011 | MULH |
| 0000001 | rs2 | rs1 | 010 | rd | 0110011 | MULHSU |
| 0000001 | rs2 | rs1 | 011 | rd | 0110011 | MULHU |
| 0000001 | rs2 | rs1 | 100 | rd | 0110011 | DIV |
| 0000001 | rs2 | rs1 | 101 | rd | 0110011 | DIVU |
| 0000001 | rs2 | rs1 | 110 | rd | 0110011 | REM |
| 0000001 | rs2 | rs1 | 111 | rd | 0110011 | REMU |

2. I-type (immediate-type) instructions: These instructions have one immediate value and one register operand. Examples include ADDI, SLTI, ANDI, ORI, XORI, SLLI, SRLI, and SRAI.

 


Figure 02: I-type instruction encoding format

Here, imm is a 12-bit immediate value, rs1 is the source register, funct3 is a function code that identifies the specific I-type instruction, rd is the destination register where the result is stored, and opcode is the operation code that identifies the type of instruction.

The instruction performs the operation specified by funct3 on the value stored in the source register rs1 and the immediate value imm. The result of the operation is stored in the destination register rd. The specific operation performed by the instruction depends on the function code funct3.

| | | | | | | |
|-----------|-------|-----|-----|----|---------|-------|
| imm[11:0] | | rs1 | 000 | rd | 0000011 | LB |
| imm[11:0] | | rs1 | 001 | rd | 0000011 | LH |
| imm[11:0] | | rs1 | 010 | rd | 0000011 | LW |
| imm[11:0] | | rs1 | 100 | rd | 0000011 | LBU |
| imm[11:0] | | rs1 | 101 | rd | 0000011 | LHU |
| imm[11:0] | | rs1 | 000 | rd | 0010011 | ADDI |
| imm[11:0] | | rs1 | 010 | rd | 0010011 | SLTI |
| imm[11:0] | | rs1 | 011 | rd | 0010011 | SLTIU |
| imm[11:0] | | rs1 | 100 | rd | 0010011 | XORI |
| imm[11:0] | | rs1 | 110 | rd | 0010011 | ORI |
| imm[11:0] | | rs1 | 111 | rd | 0010011 | ANDI |
| 0000000 | shamt | rs1 | 001 | rd | 0010011 | SLLI |
| 0000000 | shamt | rs1 | 101 | rd | 0010011 | SRLI |
| 0100000 | shamt | rs1 | 101 | rd | 0010011 | SRAI |
| imm[11:0] | | rs1 | 000 | rd | 1100111 | JALR |

3. S-type (store-type) instructions: These instructions store a value from a register into memory with an offset. Examples include SB, SH, and SW.

 


Figure 03: S-type instruction encoding format

Here, imm is a 12-bit immediate value used as an offset to access memory, rs1 is the base register used to calculate the memory address, rs2 is the source register whose value needs to be stored in memory, and funct3 identifies the specific store operation.

When executed, the S-type instruction calculates the memory address by adding the 12-bit immediate value imm to the value of register rs1. It then stores the value of register rs2 into the memory location specified by the calculated address. The specific store operation is determined by the funct3 field, which can be used to specify the byte size of the store operation, and can have values such as 000 for storing a byte, 001 for storing a halfword (2 bytes), or 010 for storing a word (4 bytes).

| | | | | | | |
|-----------|-----|-----|-----|----------|---------|----|
| imm[11:5] | rs2 | rs1 | 000 | imm[4:0] | 0100011 | SB |
| imm[11:5] | rs2 | rs1 | 001 | imm[4:0] | 0100011 | SH |
| imm[11:5] | rs2 | rs1 | 010 | imm[4:0] | 0100011 | SW |

4. U-type (upper immediate) instructions: These instructions load a 20-bit immediate value into a register. Examples include LUI and AUIPC.

 


Figure 04: U-type instruction encoding format

Here, imm is a 20-bit immediate value, rd is the destination register where the immediate value is loaded, and opcode is the operation code that identifies the specific U-type instruction.

When executed, the U-type instruction loads the 20-bit immediate value imm into register rd. The immediate value is zero-extended to 32 bits before being stored in the register. Since the immediate value is 20 bits, it cannot represent the entire 32-bit address space. To load a full 32-bit address, the U-type instruction is typically combined with a lower 12-bit immediate value specified in an I-type instruction, using a special encoding called the UJ-type (unconditional jump-type) instruction.

| | | | |
|------------|----|---------|-------|
| imm[31:12] | rd | 0110111 | LUI |
| imm[31:12] | rd | 0010111 | AUIPC |

5. B-type (branch-type) instructions: These instructions perform conditional branches based on the comparison of two register values. Examples include BEQ, BNE, BLT, BGE, BLTU, and BGEU.

 


Figure 05: B-type instruction encoding format

Here, rs1 and rs2 are the two source registers, funct3 is a function code that identifies the specific B-type instruction, opcode is the operation code that identifies the type of instruction, and imm is a 13-bit immediate value that encodes the branch offset.

The immediate value is constructed from three fields: the 1-bit imm[12] field, which is used to construct the top bit of the 13-bit immediate value; the 6-bit imm[10:5] field, which is used to construct bits 4-9 of the 13-bit immediate value; and the 4-bit imm[4:1|11] field, which is used to construct bits 0-3 and 12 of the 13-bit immediate value.

The rs1 and rs2 registers are compared based on the specific function code funct3. If the comparison is true, then the program counter is updated to the target address computed from the relative branch offset. If the comparison is false, the program counter is incremented to the next sequential instruction.

| | | | | | | |
|--------------|-----|-----|-----|-------------|---------|------|
| imm[12:10:5] | rs2 | rs1 | 000 | imm[4:1:11] | 1100011 | BEQ |
| imm[12:10:5] | rs2 | rs1 | 001 | imm[4:1:11] | 1100011 | BNE |
| imm[12:10:5] | rs2 | rs1 | 100 | imm[4:1:11] | 1100011 | BLT |
| imm[12:10:5] | rs2 | rs1 | 101 | imm[4:1:11] | 1100011 | BGE |
| imm[12:10:5] | rs2 | rs1 | 110 | imm[4:1:11] | 1100011 | BLTU |
| imm[12:10:5] | rs2 | rs1 | 111 | imm[4:1:11] | 1100011 | BGEU |

6. J-type (jump-type) instructions: These instructions perform unconditional jumps and jump with a link (i.e., save the address of the next instruction to be executed). Examples include JAL and JALR.

 


Figure 06: J-type instruction encoding format

Here, rd is the destination register, which is used to store the return address of the jump instruction. The immediate value is added to the current program counter (PC) value to compute the target address. The immediate value is then shifted left by 1 bit to adjust for the fact that RISC-V instructions are 32 bits long and the target address must be aligned to a 32-bit boundary.

After the jump instruction is executed, the PC is set to the target address computed from the immediate value, with the least-significant bit set to zero to ensure that the target address is aligned to a 32-bit boundary. The rd register is used to store the return address of the jump instruction, which is the address of the instruction following the jump instruction.



Instructions and their opcodes

R-Type instructions

| Instruction | Description | Opcode | func3 | func7 |
|-------------|---|---------|-------|---------|
| ADD | ADD the value in rs1 and rs2 value and put it into rd | 0110011 | 000 | 0000000 |
| SUB | SUBTRACT the value in rs1 and rs2 value and put it into rd | 0110011 | 000 | 0100000 |
| SLL | Shift Left Logical (rs1 value by rs2 amount and put it to rd) | 0110011 | 001 | 0000000 |
| SLT | Set less than (if rs1 value less than rs2 value then put 1 to the rd register else 0 to the rd register) | 0110011 | 010 | 0000000 |
| SLTU | Set less than Unsigned (if rs1 value less than rs2 value then put 1 to the rd register else 0 to the rd register) | 0110011 | 011 | 0000000 |
| XOR | XOR the value in rs1 and rs2 value and put it into rd | 0110011 | 100 | 0000000 |
| SRL | Shift Right Logical (rs1 value by rs2 amount and put it to rd) | 0110011 | 101 | 0000000 |
| SRA | Shift Right Arithmetic (rs1 value by rs2 amount and put it to rd) | 0110011 | 101 | 0100000 |
| OR | OR the value in rs1 and rs2 value and put it into rd | 0110011 | 110 | 0000000 |
| AND | AND the value in rs1 and rs2 value and put it into rd | 0110011 | 111 | 0000000 |

| | | | | |
|--------|--|---------|-----|---------|
| MUL | Multiplication | 0110011 | 000 | 0000001 |
| MULH | Returns upper 32-bits of signed x signed (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 001 | 0000001 |
| MULHSU | Returns upper 32-bits of signed x unsigned (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 010 | 0000001 |
| MULHU | Returns upper 32-bits of unsigned x unsigned (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 011 | 0000001 |
| DIV | Signed Integer division (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 100 | 0000001 |
| DIVU | Unsigned Integer division (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 101 | 0000001 |
| REM | Signed remainder of integer division (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 110 | 0000001 |
| REMU | Unsigned remainder of integer division (use rs1 value and the rs2 value and put the answer to the rd register) | 0110011 | 111 | 0000001 |

I-Type instructions

| Instruction | Description | Opcode | func3 | func7 |
|-------------|--|---------|-------|---------|
| LB | Load Byte to rd register (signed extended) | 0000011 | 000 | |
| LH | Load 2 Bytes to rd register (signed extended) | 0000011 | 001 | |
| LW | Load Word to rd register (signed extended) | 0000011 | 010 | |
| LBU | Load Byte to rd register (zero extended) | 0000011 | 100 | |
| LHU | Load 2 Bytes to rd register (zero extended) | 0000011 | 101 | |
| ADDI | ADD immediate value and value of rs1 and put result to rd register | 0010011 | 000 | |
| SLLI | Shift Left Logical with Immediate (shift rs1 value by immediate amount) | 0010011 | 001 | 0000000 |
| SLTI | if immediate value is less than value of rs1 put 1 to rd register otherwise put 0 | 0010011 | 010 | |
| SLTIU | if immediate value is less than value of rs1 put 1 to rd register otherwise put 0 (unsigned) | 0010011 | 011 | |
| XORI | XOR immediate value and value of rs1 and put result to rd register | 0010011 | 100 | |
| SRLI | Shift Right Logical with Immediate (shift rs1 value by immediate amount) | 0010011 | 101 | 0000000 |
| SRAI | Shift Right Arithmetic Immediate (shift rs1 value by immediate amount) | 0010011 | 101 | 0100000 |
| ORI | OR immediate value and value of rs1 and put result to rd register | 0010011 | 110 | |
| ANDI | AND immediate value and value of rs1 and put result to rd register | 0010011 | 111 | |
| JALR | Jump and Link Register | 1100111 | | |

S-Type instructions

| Instruction | Description | Opcode | func3 | func7 |
|-------------|--|---------|-------|-------|
| SB | Store Byte rs2 reg value, base is in rs1 address and the offset taken from the immediate value | 0100011 | 000 | |
| SH | rs2 reg value, base is in rs1 address and the offset taken from the immediate value | 0100011 | 001 | |
| SW | rs2 reg value, base is in rs1 address and the offset taken from the immediate value | 0100011 | 010 | |
| SBU | Store unsigned Byte | 0100011 | 100 | |
| SHU | Store unsigned half word | 0100011 | 101 | |

U-Type instructions

| Instruction | Description | Opcode | func3 | func7 |
|-------------|--|---------|-------|-------|
| AUIPC | Add upper immediate to PC and put to rd register | 0010011 | | |
| LUI | Load Upper Immediate (puts the immediate value with 12 zeros at the end and put it into rd register) | 0110111 | | |

B-Type instructions

| Instruction | Description | Opcode | func3 | func7 |
|-------------|--|---------|-------|-------|
| BEQ | Branch if equal (if values in rs1 and rs2 are equal jump to the offset) | 1100011 | 000 | |
| BNE | Branch if not equal (if values in rs1 and rs2 are not equal jump to the offset) | 1100011 | 001 | |
| BLT | Branch if lower than (if values in rs1 < rs2 jump to the offset) | 1100011 | 100 | |
| BGE | Branch if greater than or equal (if values in rs1 > rs2 jump to the offset) | 1100011 | 101 | |
| BLTU | Branch if lower than, unsigned (if values in rs1 < rs2 jump to the offset) | 1100011 | 110 | |
| BGEU | Branch greater than or equal, unsigned (if values in rs1 > rs2 jump to the offset) | 1100011 | 111 | |

J-Type instructions and other instructions

| Instruction | Description | Opcode | func3 | func7 |
|-------------|---|---------|-------|-------|
| JAL | Jump and Link (Jumps to the address in rs1 and put the current PC to the rd register) | 1101111 | | |
| FENCE | Fence - This to ensure all the operation before FENCE observed before operation after the Fence | 0001111 | 000 | |
| FENCE.I | Fence Instruction | 0001111 | 001 | |

Pipeline diagram with datapath and control

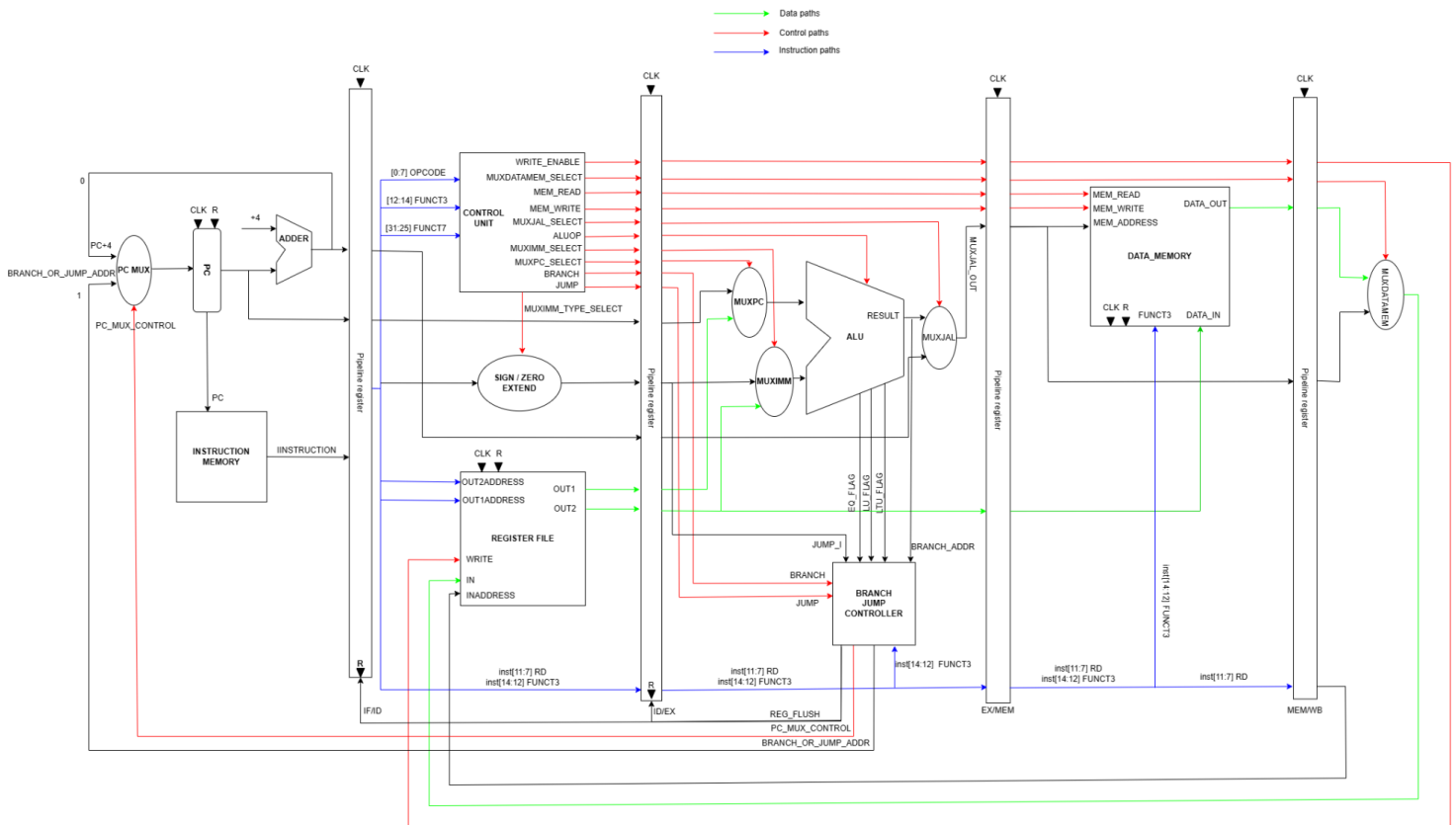


Figure 07: Pipeline diagram with datapath and control

In case of not clear enough to observe above **FIGURE 07** - [Pipeline diagram with datapath and control path](#)

Main units of the processor

1. Instruction Memory

 


Figure 08: Instruction Memory

Inputs

1. PC - the memory address of the next instruction to be executed in a computer program.

Outputs

1. INSTRUCTION - 32-bit Instruction

Design Decision

So far implemented 1024*8 bits memory. Which can hold 256 instructions. If necessary we can increase the size of the instruction memory.

Instructions were hardcoded in this instruction memory for the testing purpose,

```
{memory_array[10'd3], memory_array[10'd2], memory_array[10'd1], memory_array[10'd0]} = 32'b0000000100000001000000000010011; // addi x1, x0, 10
{memory_array[10'd7], memory_array[10'd6], memory_array[10'd5], memory_array[10'd4]} = 32'b0000001000000010000000000010011; // addi x2, x0, 20
{memory_array[10'd11], memory_array[10'd10], memory_array[10'd9], memory_array[10'd8]} = 32'b00000011000100010000000000110011; // add x3, x1, x2
{memory_array[10'd15], memory_array[10'd14], memory_array[10'd13], memory_array[10'd12]} = 32'b00000000000000110000000000100011; // sw x3, 0(x0)
```

Result of the instruction testbed,

```
shamod@J-A-R-V-I-S:/mnt/d/Semester 6/CO502 Advanced Computer Architecture/e18-co502-RISCV-Pipeline-CPU-Implimentation-Group4/cpu/Instruction_Memory$ vvp o.vvp
VCD info: dumpfile instruction_memory_tb.vcd opened for output.
Instruction at address 0: 0000000100000001000000000010011
Instruction at address 4: 0000001000000010000000000010011
Instruction at address 8: 00000011000100010000000000110011
Instruction at address 12: 00000000000000110000000000100011
```

2. Control Unit

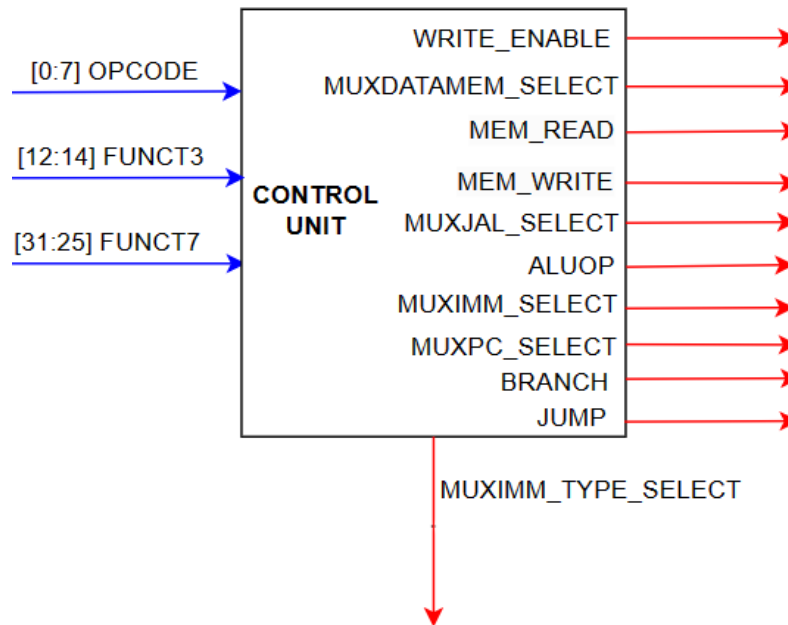


Figure 09: Control Unit

Inputs

1. OPCODE

An OPCODE, short for "operation code," is a binary code that specifies the operation to be performed by a processor or microcontroller in order to execute a particular instruction.

2. FUNCT3

FUNCT3 (short for function 3) is a field in the instruction format that specifies a subset of operations that can be performed by an instruction.

3. FUNCT7

FUNCT7 (short for function 7) is a field in the instruction format that provides additional information about the operation to be performed by an instruction.

Outputs - Control signals

1. WRITE_ENABLE:

1 bit signal. This is the control signal that determines whether data can be written into the register.

When,

WRITE_ENABLE=1 → Enables the write operation to the register file
WRITE_ENABLE=0 → Disables the write operation to the register file

2. MUXDATAMEM_SELECT:

1 bit signal. This is the select signal for MUXDATAMEM which is used to select between MUXJAL_OUT and data memory output (DATA_OUT). Then the selected data is directed to the register file.

When,

MUXDATAMEM_SELECT=1 → DATA_OUT
MUXDATAMEM_SELECT=0 → MUXJAL_OUT

3. MEM_READ:

1 bit signal. This is the control signal that enables the output data from the memory unit. When the MEM_READ signal is high, the memory unit is instructed to output data (DATA_OUT) from the specified address, which is provided on the address lines (MEM_ADDRESS).

When,

MEM_READ=1 → Enables the read operation from the data memory
MEM_READ=0 → Disables the read operation from the data memory

4. MEM_WRITE:

1 bit signal. This is the control signal that enables the input data to be written into the memory unit. When the MEM_WRITE signal is high, the memory unit is instructed to write the data provided on the data lines (DATA_IN) to the specified address on the address lines (MEM_ADDRESS).

When,

MEM_WRITE=1 → Enables the write operation to the data memory
MEM_WRITE=0 → Disables the write operation to the data memory

5. MUXJAL_SELECT:

1 bit signal. This is the select signal for the MUXJAL multiplexer which is used to select between ALU_RESULT and current PC+4 value.

When,

MUXJAL_SELECT=1 → PC+4
MUXJAL_SELECT=0 → ALU_RESULT

6. ALUOP:

5-bit signal for ALU. This signal specifies the arithmetic or logical operation to be performed by the ALU. It selects one of several operations that the ALU can perform, such as addition, subtraction, multiplication, bitwise AND, OR, XOR, and shift operations.

7. MUXPC_SELECT:

1 bit signal. This is the select signal for MUXPC, which is used to select between register file output (REGOUT1) and PC value. Then the selected data is directed to the ALU for its operations.

When,

MUXPC_SELECT=1 → PC

MUXPC_SELECT=0 → REGOUT1

8. MUXIMM_SELECT:

1 bit signal. This is the select signal for MUXIMM, which is used to select between immediate value and register file output (REGOUT2). Then the selected data is directed to the ALU for its operations.

When,

MUXIMM_SELECT=1 → IMMEDIATE VALUE

MUXIMM_SELECT=0 → REGOUT2

9. MUXIMMTYPE_SELECT:

3 bit signal. This is the select signal for MUXIMMTYPE, which is used to select between I_IMM, S_IMM, B_IMM, U_IMM, J_IMM. Then the selected data is directed to the MUXIMM.

When,

MUXIMMTYPE_SELECT=000 → I_IMM

MUXIMMTYPE_SELECT=001 → S_IMM

MUXIMMTYPE_SELECT=010 → U_IMM

MUXIMMTYPE_SELECT=011 → B_IMM

MUXIMMTYPE_SELECT=100 → J_IMM

10. BRANCH and JUMP:

1-bit signals. These signals are used in the BRANCH JUMP CONTROLLER in order to distinguish whether the instruction is a branch or a jump. The BRANCH signal is used to conditionally execute a set of instructions based on a particular condition. The JUMP signal is used to unconditionally jump to a specific instruction address.

When,

BRANCH=1 → Enables branch operation

BRANCH=0 → Disables branch operation

JUMP=1 → Enables jump operation

JUMP=0 → Disables jump operation

Note:

- Though the above diagram displays the parts of the decoded instruction (OPCODE, FUNCT3, FUNCT7) which are used in the control unit as inputs to determine the control signals; in our implementation, we have done the decoding inside the control unit module. Hence, we have used the whole 32-bit INSTRUCTION as input to the control unit.
- All the control signals of the control unit are indicated in red in the datapath and control diagram.

Design decisions

As the first step we have decoded the instruction and extracted the OPCODE, FUNCT3 and FUNCT7.

We can observe that, for the instruction set we have considered, we only need the 0th and 5th bits of FUNCT7. But considering further expansion of our instruction set, we have used all the 7-bits of FUNCT7 in our implementation.

When we consider the R type instructions their OPCODEs are the same. They are differentiated using FUNCT3 and FUNCT7. All the control signals are the same for these instructions except for the ALUOP. Since, we have used a nested case structure to implement this. We have defined all the control signals except ALUOP in the outer case as they are the same for all R type instructions and ALUOP was defined for each instruction in the inner case considering FUNCT3 and FUNCT7. This will make the code much simpler and easy to understand. The same thing was done for I type instructions as well.

For load and store instructions the control unit generates the same control signals, whether the instruction is a full word, half word or a byte. These instructions are controlled in the memory access stage using the FUNCT3 field.

The below table consists of all the control signals for each instruction,

Control logic truth table (Considering both control unit and branch/jump controller unit)

| INSTRUC TION | ALUOP | EQ_ F L A G | LT_ F L A G | LTU_ F L A G | PC MUX_ SEL | MUX IMM_ TYPE_ SEL | MUX PC_ SEL | MUX IMM_ SEL | MUX JAL_ SEL | MUXDATA MEM_SEL | WRITE_ ENABLE | M E M _ R E A D | M E M _ W R I T E | B R A N C H | J U M P |
|-----------------|-------|-------------------------|-------------------------|--------------------------|-------------------|-----------------------------|-------------------|--------------------|--------------------|--------------------|------------------|--------------------------------------|---|----------------------------|------------------|
| ADD | ADD | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |

| | | | | | | | | | | | | | | | |
|--------|--------|---|---|---|-----|-------|-----|-----|------|--------|---|---|---|---|---|
| SUB | SUB | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SLL | SLL | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SLT | SLT | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SLTU | SLTU | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| XOR | XOR | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SRL | SRL | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SRA | SRA | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| OR | OR | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| AND | AND | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| MUL | MUL | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| MULH | MULH | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| MULHSU | MULHSU | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| MULHU | MULHU | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| DIV | DIV | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| DIVU | DIVU | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| REM | REM | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| REMU | REMU | * | * | * | +4 | * | Reg | Reg | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| LB | ADD | * | * | * | +4 | I_Imm | Reg | Imm | ALU | Mem | 1 | 1 | 0 | 0 | 0 |
| LH | ADD | * | * | * | +4 | I_Imm | Reg | Imm | ALU | Mem | 1 | 1 | 0 | 0 | 0 |
| LW | ADD | * | * | * | +4 | I_Imm | Reg | Imm | ALU | Mem | 1 | 1 | 0 | 0 | 0 |
| LBU | ADD | * | * | * | +4 | I_Imm | Reg | Imm | ALU | Mem | 1 | 1 | 0 | 0 | 0 |
| LHU | ADD | * | * | * | +4 | I_Imm | Reg | Imm | ALU | Mem | 1 | 1 | 0 | 0 | 0 |
| ADDI | ADD | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SLLI | SLL | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SLTI | SLT | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SLTIU | SLTU | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| XORI | XOR | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| SRLI | SRL | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| ORI | OR | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| ANDI | AND | * | * | * | +4 | I_Imm | Reg | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| JALR | ADD | * | * | * | ALU | I_Imm | Reg | Imm | PC+4 | MUXJAL | 1 | 0 | 0 | 0 | 1 |
| SB | ADD | * | * | * | +4 | S_Imm | Reg | Imm | ALU | * | 0 | 0 | 1 | 0 | 0 |
| SH | ADD | * | * | * | +4 | S_Imm | Reg | Imm | ALU | * | 0 | 0 | 1 | 0 | 0 |
| SW | ADD | * | * | * | +4 | S_Imm | Reg | Imm | ALU | * | 0 | 0 | 1 | 0 | 0 |

| | | | | | | | | | | | | | | | |
|-------|---------|---|---|---|-----|-------|-----|-----|------|--------|---|---|---|---|---|
| SBU | ADD | * | * | * | +4 | S_Imm | Reg | Imm | ALU | * | 0 | 0 | 1 | 0 | 0 |
| SHU | ADD | * | * | * | +4 | S_Imm | Reg | Imm | ALU | * | 0 | 0 | 1 | 0 | 0 |
| AUIPC | ADD | * | * | * | +4 | U_Imm | PC | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| LUI | FORWARD | * | * | * | +4 | U_Imm | * | Imm | ALU | MUXJAL | 1 | 0 | 0 | 0 | 0 |
| BEQ | SUB | 0 | * | * | +4 | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BEQ | SUB | 1 | * | * | ALU | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BNE | SUB | 0 | * | * | ALU | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BNE | SUB | 1 | * | * | +4 | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BLT | SUB | * | 1 | * | ALU | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BGE | SUB | * | 0 | * | ALU | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BLTU | SUB | * | * | 1 | ALU | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| BGEU | SUB | * | * | 0 | ALU | B_Imm | PC | Imm | ALU | * | 0 | 0 | 0 | 1 | 0 |
| JAL | ADD | * | * | * | ALU | J_Imm | PC | Imm | PC+4 | MUXJAL | 1 | 0 | 0 | 0 | 1 |

Note: Above table is colored by considering the type of instruction.

Timing

As the first step we have decoded the instruction and extracted the OPCODE, FUNCT3 and FUNCT7. For this we didn't add a delay. As it is just an asynchronous wire operation, the time delay for this is very low.

For all instructions we have introduced #1 time unit delay for generating control signals to represent combinational logic delays.

| Description | Delay |
|----------------------------|-------|
| Combinational logic delays | #1 |

3. Register File

The purpose of the register file is to store output values generated by the ALU, and to supply the ALU's inputs with operands.

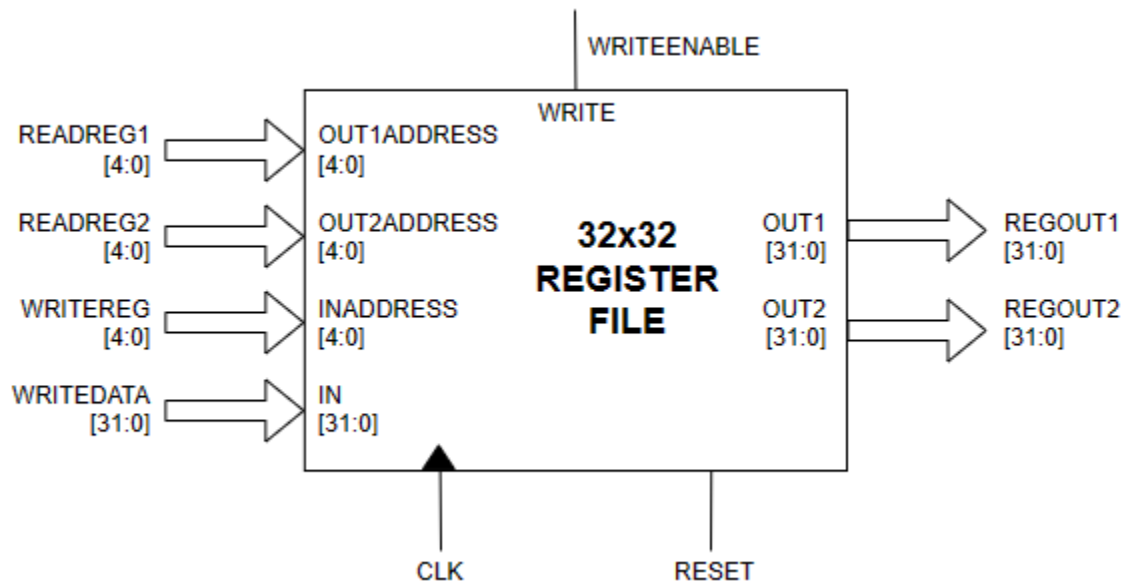


Figure 10: Register File

Inputs

1. CLK

In a register file, the clock signal is used to trigger the read or write operations to the registers.

2. RESET

The RESET signal is a read control signal that is used to enable a read operation from the register file.

3. OUT1ADDRESS and OUT2ADDRESS

These are address signals that are used to specify the register addresses for a read operation.

4. WRITE

This is used to enable a write operation to the register file.

5. IN

This is used to specify the data value to be written to a register in the register file during a write operation.

6. INADDRESS

This is used to specify the address of the register to be written during a write operation.

Outputs

1. OUT1 and OUT2

OUT1 and OUT2 are typically used in the context of an arithmetic or logic operation in a computer system. They represent the two data operands that are being used in the operation.

Design decisions

- 32x32 register file (Can store thirty two 32-bit values, register0 - register31).
- Contains one 32-bit data input port (IN) and two 32-bit output ports (OUT1 and OUT2).
- Three 5-bit address ports (INADDRESS, OUT1ADDRESS, OUT2ADDRESS) are included to specify which register is reading or writing.
- Control port WRITE is used to accommodate the WRITEENABLE control signal.
- As the register file is a sequential unit, CLOCK and RESET signals are used for synchronization.
- The port IN represents the data input, with INADDRESS providing the register number to store data in. The ports OUT1 and OUT2 are parallel data outputs, where OUT1ADDRESS and OUT2ADDRESS respectively provide the register numbers where data is retrieved from.

Read operation

- Registers identified by OUT1ADDRESS and OUT2ADDRESS are used to read asynchronously and the values are loaded to OUT1 and OUT2 respectively.

Write operation


- Writing to the register file is done synchronously.
- When the WRITEENABLE signal at the write port is set high, the rising edge of CLOCK makes the data present on the IN port to be written to the input register specified by the INADDRESS.
- Register file reset happens synchronously at the positive edge of the clock if the RESET signal is high. In a reset event, all registers are cleared (written zero).

Timing

To simulate the register file read and write latencies realistically, artificial delays of two time units (#2) for register reading and one time unit (#1) for writing operations including reset were added.

| Description | Delay |
|-----------------|-------|
| Read operation | #2 |
| Write operation | #1 |
| Reset | #1 |

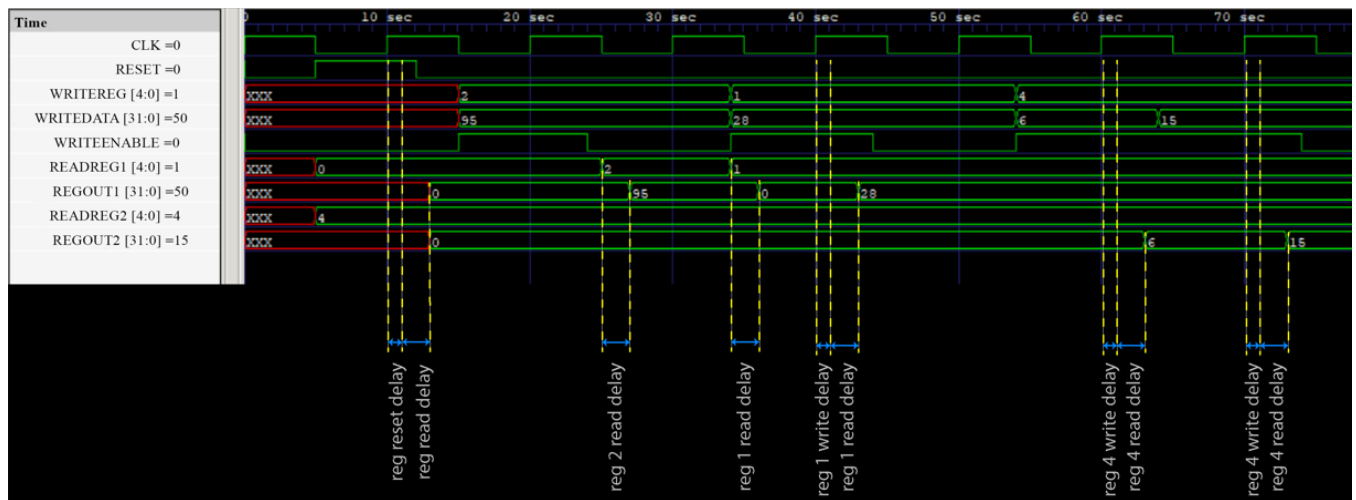Timing diagram for register file testbench generated using GTKWave,



4. ALU

This is the part of the computer processor which performs arithmetic and logic operations on numbers, e.g. addition, subtraction, etc.

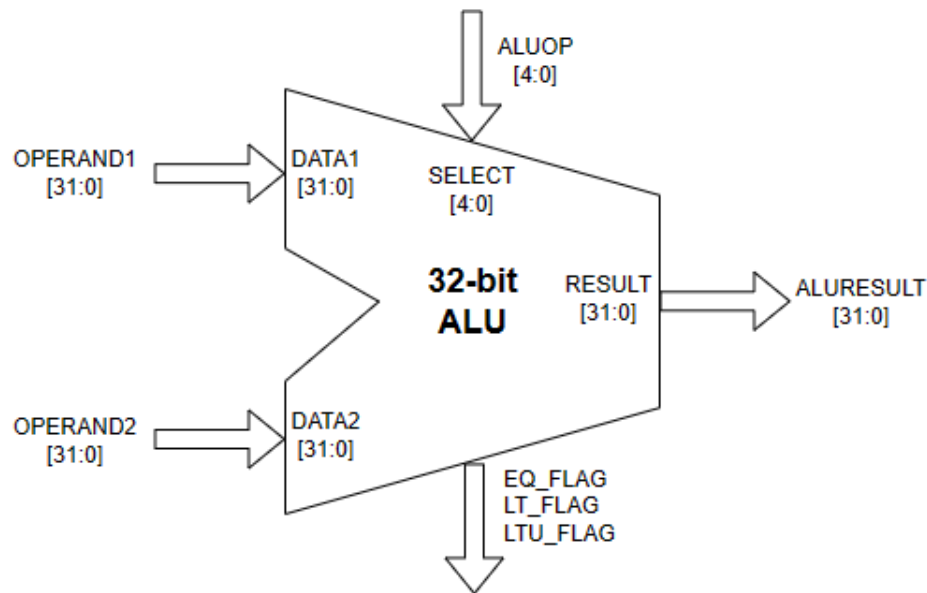


Figure 11: Interfaces of the ALU

Inputs

1. DATA1 and DATA2

Two 32-bit input ports for operands

2. SELECT

5-bit control input port which is used to pick the required function inside the ALU. As there are 18 functions in our ALU, 5-bit is the minimum required size for the SELECT input.

Outputs

1. RESULT

32-bit output port

2. EQ_FLAG (Equal flag)

1-bit output signal used to notify whether DATA1=DATA2 or not. Implemented using the help of ALU SUB operation.

When,

$$\text{DATA1}=\text{DATA2} \rightarrow \text{EQ_FLAG} = 1$$

$$\text{DATA1} \neq \text{DATA2} \rightarrow \text{EQ_FLAG} = 0$$

3. LT_FLAG (Less than flag)

1-bit output signal used to notify whether $\text{DATA1} < \text{DATA2}$ or not. Implemented using the help of ALU SUB operation.

When,

$$\text{DATA1} < \text{DATA2} \rightarrow \text{LT_FLAG} = 1$$

$$\text{DATA1} \geq \text{DATA2} \rightarrow \text{LT_FLAG} = 0$$

4. LTU_FLAG (Less than unsigned flag)

1-bit output signal used to notify whether $\text{DATA1} < \text{DATA2}$ or not for unsigned data. Implemented using the help of ALU SLTU operation. Any bit of the RESULT of SLTU operation can be considered (In our implementation, we have considered the zeroth bit of the RESULT of SLTU operation).

When,

$$\text{unsigned}(\text{DATA1}) < \text{unsigned}(\text{DATA2}) \rightarrow \text{LTU_FLAG} = 1$$

$$\text{unsigned}(\text{DATA1}) \geq \text{unsigned}(\text{DATA2}) \rightarrow \text{LTU_FLAG} = 0$$

Design decisions

- 32-bit ALU. Hence it works with 32-bit operands. This means that all data inputs and outputs of the ALU are 32-bit values.
- Contains two 32-bit input ports for operands (DATA1 and DATA2), one 32-bit output port (RESULT) and one 5-bit control port (SELECT) which is used to pick the required function inside the ALU out of the available 19 functions based on the instructions.
- As there are 19 functions in our ALU, 5-bit is used for the SELECT input which is the minimum number of bits required.
- This is a fully asynchronous module.
- RISC-V uses a reduced instruction set compared to other architectures, which means that the ALU only needs to support a smaller set of instructions. This simplifies the design and reduces the hardware resources required.
- Support for multiplication and division operations, which are essential for many applications.
- The ALU generates EQ_FLAG, LT_FLAG and LTU_FLAG control signals. These flags are used by the branch and jump controller unit to determine the next instruction to be executed.
- The ALU works as follows for each type of instruction,
 - R, I type instructions: Performs the relevant operation for each instruction (Ex: ADD, SUB)
 - Load and store instructions: Calculates the data memory address using ADD operation
 - Branch instructions: Performs the SUB operation and sets the EQ_FLAG, LT_FLAG and LTU_FLAG accordingly.

- Jump instructions: Calculates the jump address using ADD operation

Limitations

- The ALU only supports 32-bit inputs and outputs.
- Limited precision for multiplication and division operations.
- The ALU does not support floating point operations because it is designed to perform arithmetic and logical operations on binary data, which are typically represented using fixed-point or integer data types.

Timing

To simulate the ALU latencies realistically, artificial delays were added to each function as shown in the below table. For addition and subtraction, a delay of two-time units (#2) was added. As the delay for logic operations and shift operations is less compared to ADD and SUB, a delay of one-time unit (#1) was introduced. As multiplication and division are complex functions its delay is high compared to others. So, a delay of three-time units (#3) was added for multiplication and division operations.

The table below shows the 19 functions that our 32-bit ALU can perform with the relevant Unit's delay.

ALU functions

| SELECT | Function | Description | Supported Instructions | Unit's Delay |
|--------|----------|---|---|--------------|
| 00000 | FORWARD | (forward DATA2 into RESULT) DATA2 → RESULT | LUI | #1 |
| 00001 | ADD | (Add DATA1 and DATA2) DATA1 + DATA2 → RESULT | ADD, LB, LH, LW, LBU, LHU, ADDI, JAL, JALR, SB, SH, SW, SBU, SHU, AUIPC | #2 |
| 00010 | SUB | (Subtract DATA2 from DATA1) DATA1 - DATA2 → RESULT | SUB, BEQ, BNE, BLT, BGE, BLTU, BGEU | #2 |
| 00011 | SLL | (Shift left logical) DATA1 << DATA2 → RESULT | SLL, SLLI | #1 |

| | | | | |
|-------|--------|--|-------------|----|
| 00100 | SLT | (Set less than) If (\$signed(DATA1) < \$signed(DATA2)) → RESULT=32'd1 else → RESULT=32'd0 | SLT, SLTI | #1 |
| 00101 | SLTU | (Set less than unsigned) If (\$unsigned(DATA1) < \$unsigned(DATA2)) → RESULT=32'd1 else → RESULT=32'd0 | SLTU, SLTIU | #1 |
| 00110 | XOR | (Bitwise XOR on DATA1 with DATA2) DATA1 ^ DATA2 → RESULT | XOR, XORI | #1 |
| 00111 | SRL | (Shift right logical) DATA1 >> DATA2 → RESULT | SRL, SRLI | #1 |
| 01000 | SRA | (Shift right arithmetic) DATA1 >>> DATA2 → RESULT | SRA | #1 |
| 01001 | OR | (Bitwise OR on DATA1 with DATA2) DATA1 DATA2 → RESULT | OR, ORI | #1 |
| 01010 | AND | (Bitwise AND on DATA1 with DATA2) DATA1 & DATA2 → RESULT | AND, ANDI | #1 |
| 01011 | MUL | (Multiplication) DATA1 * DATA2 → RESULT | MUL | #3 |
| 01100 | MULH | (Multiplication>Returns upper 32 bits) (DATA1 * DATA2)>>32 → RESULT | MULH | #3 |
| 01101 | MULHSU | (Multiplication>Returns upper 32 bits (Signed x UnSigned)) (\$signed(DATA1) * \$unsigned(DATA2))>>32 → RESULT | MULHSU | #3 |
| 01110 | MULHU | (Multiplication>Returns upper 32 bits (UnSigned)) (\$unsigned(DATA1) * \$unsigned(DATA2))>>32 → RESULT | MULHU | #3 |
| 01111 | DIV | (Division) DATA1 / DATA2 → RESULT | DIV | #3 |
| 10000 | DIVU | (Division Unsigned) \$unsigned(DATA1) / \$unsigned(DATA2) → RESULT | DIVU | #3 |

2. Testing using testbench 2 (This is easy to understand)

```
Test case 1: Forward operation  
OPERAND1 :      20  
OPERAND2 :       2  
ALURESULT :       2  
  
Test case 2: OPERAND1 + OPERAND2  
OPERAND1 :      20  
OPERAND2 :       2  
ALURESULT :     22  
  
Test case 3: OPERAND1 - OPERAND2  
OPERAND1 :      20  
OPERAND2 :       2  
ALURESULT :     18  
  
Test case 4: OPERAND1 << OPERAND2  
OPERAND1 : 000000000000000000000000000010100  
OPERAND2 :          2  
ALURESULT : 00000000000000000000000001010000  
  
Test case 5: Set less than (When OPERAND1 > OPERAND2)  
OPERAND1 :      20  
OPERAND2 :       2  
ALURESULT :       0  
  
Test case 6: Set less than (When OPERAND1 < OPERAND2)  
OPERAND1 :       2  
OPERAND2 :     20  
ALURESULT :       1
```

Note: As there are many test cases, all the test case results are not shown in the report. But we have implemented them in the ALU test bench.

5. Branch-Jump Controller

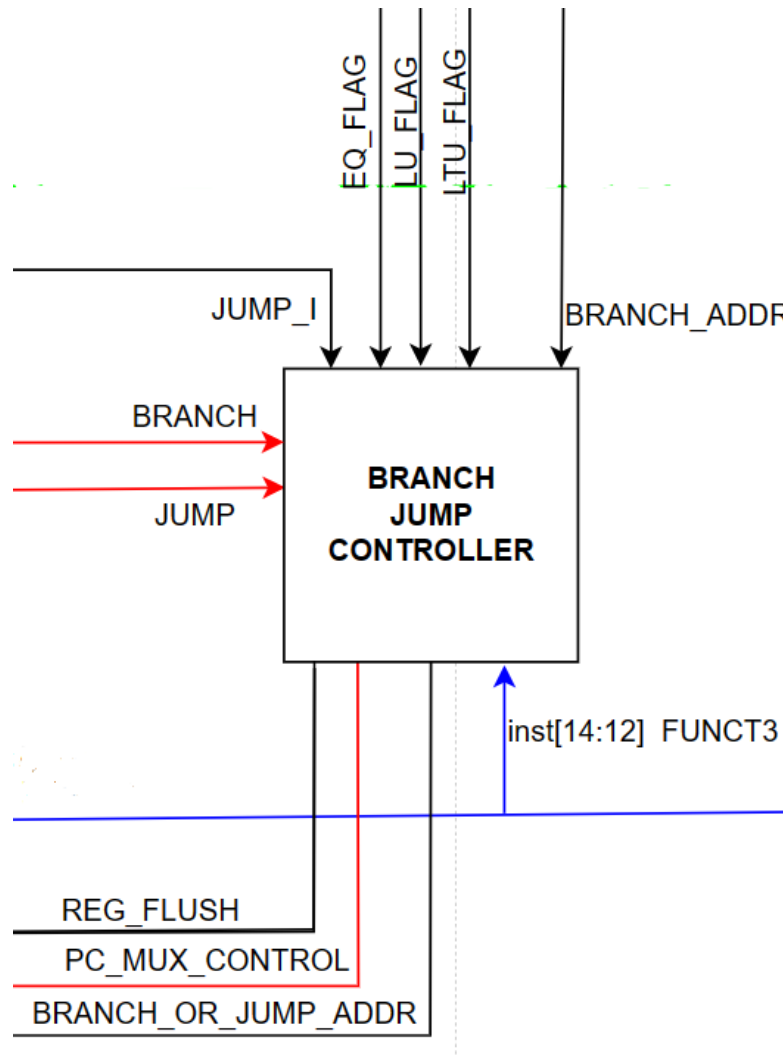


Figure 12: Branch Jump Controller

Inputs

1. BRANCH

The BRANCH input is a signal that indicates whether a branch instruction has been executed.

2. JUMP

The JUMP input is a signal that indicates whether a jump instruction has been executed.

3. FUNCT3

Used to distinguish the condition of the branch instruction (Ex: Branch Less Than, Branch Greater Than or Equal, Branch Less Than Unsigned, etc)

4. EQ_FLAG (Equal flag)

1-bit input signal used to notify whether DATA1=DATA2 or not from ALU.

5. LT_FLAG (Less than flag)

1-bit input signal used to notify whether DATA1<DATA2 or not from ALU.

6. LTU_FLAG (Less than unsigned flag)

1-bit input signal used to notify whether DATA1<DATA2 or not for unsigned data from ALU.

7. JUMP_I

32 bit jump immediate value from sign and zero extend unit

8. BRANCH_ADDR

32 bit branch address which was calculated using the adder in ALU.

Outputs

1. PC_MUX_CONTROL

This is used in PC MUX as the select bit to choose the next PC value

2. BRANCH_OR_JUMP_ADDR

This contains the target address of the Branch/ Jump instruction that has been executed.

3. REG_FLUSH

This signal is used to clear fetched data from the pipeline registers (IF/ID Register and ID/EX Register) when branch or jump occurs.

Design Decisions

Delays- correct control signals will be available after a single time unit once the all necessary signals are received.

| Instruction | Input | | | | | | | Output | | |
|-------------|--------|---|---|--------|------|---------|---------|----------|----------------|-----------|
| | FUNCT3 | | | BRANCH | JUMP | EQ_FLAG | LT_FLAG | LTU_FLAG | PC_MUX_CONTROL | REG_FLUSH |
| JAL | NA | | | 0 | 1 | NA | NA | NA | 1 | 1 |
| BEQ | 0 | 0 | 0 | 1 | 0 | 1 | NA | NA | 1 | 1 |
| BNE | 0 | 0 | 1 | 1 | 0 | 0 | NA | NA | 1 | 1 |
| BLT | 1 | 0 | 0 | 1 | 0 | 0 | 1 | NA | 1 | 1 |
| BGE | 1 | 0 | 1 | 1 | 0 | NA | 0 | NA | 1 | 1 |
| BLTU | 1 | 1 | 0 | 1 | 0 | 0 | NA | 1 | 1 | 1 |
| BGEU | 1 | 1 | 1 | 1 | 0 | NA | NA | 0 | 1 | 1 |

Output Signals According to Branch and Jump instructions to take the Branch or Jump

- Other Instructions and other combinations for above instructions (not affect if the necessary signal values are satisfied)

PC_MUX_CONTROL = 0

REG_FLUSH = 0

Testing Results for jump control unit:-

```
shamod@J-A-R-V-I-S:/mnt/d/Semester 6/C0502 Advanced Computer Architecture/e18-co502-RISC-V-Pipeline-CPU-Implimentation-Group4/cpu/Jump_Controller$ iverilog -o o.vvp Jump_Controller_tb.v
shamod@J-A-R-V-I-S:/mnt/d/Semester 6/C0502 Advanced Computer Architecture/e18-co502-RISC-V-Pipeline-CPU-Implimentation-Group4/cpu/Jump_Controller$ vvp o.vvp
Test 1 ( JUMP ): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 0, JUMP = 1, EQ_FLAG = x, LT_FLAG = x, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00002000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 2 (BEQ -T): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 1, LT_FLAG = x, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 3 (BEQ -F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = x, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 4 (BNE -T): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = x, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 5 (BNE -F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 1, LT_FLAG = x, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 6 (BLT -T): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = 1, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 7 (BLT -F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 1, LT_FLAG = 1, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 8 (BLT -F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 1, LT_FLAG = 0, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 9 (BGE -T): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = x, LT_FLAG = 0, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 10 (BGE -F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = x, LT_FLAG = 1, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 11 (BLTU-T): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = x, LTU_FLAG = 1, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 12 (BLTU-F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = x, LTU_FLAG = 0, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 13 (BLTU-F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 1, LT_FLAG = x, LTU_FLAG = 1, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 14 (BGEU-T): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = x, LTU_FLAG = 0, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 1, REG_FLUSH = 1
Test 15 (BGEU-F): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 1, JUMP = 0, EQ_FLAG = 0, LT_FLAG = x, LTU_FLAG = 1, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
Test 16 (OTHERS): BRANCH_ADDR = 00001000, JUMP_I = 00002000, BRANCH = 0, JUMP = 0, EQ_FLAG = x, LT_FLAG = x, LTU_FLAG = x, BRANCH_OR_JUMP_ADDR = 00001000, PC_MUX_CONTROL = 0, REG_FLUSH = 0
shamod@J-A-R-V-I-S:/mnt/d/Semester 6/C0502 Advanced Computer Architecture/e18-co502-RISC-V-Pipeline-CPU-Implimentation-Group4/cpu/Jump_Controller$
```

6. Memory

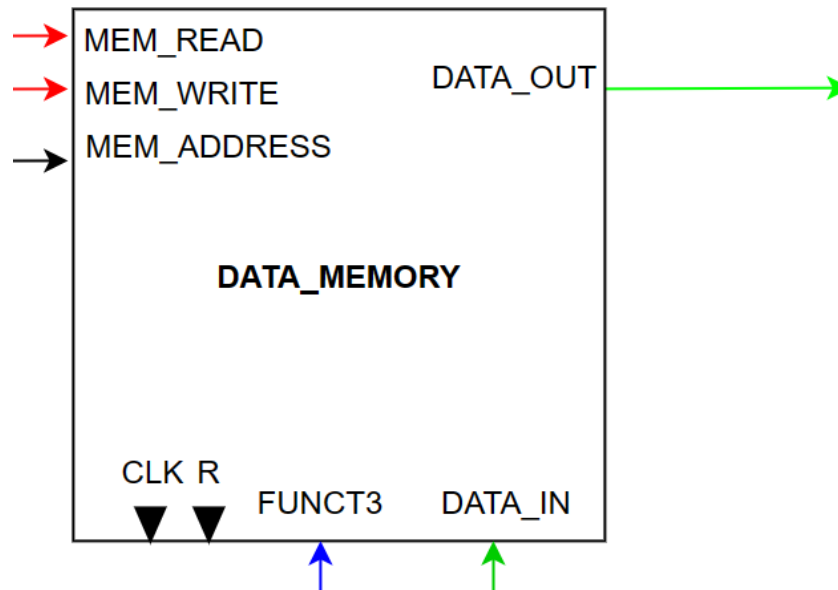


Figure 13: Memory

Inputs

1. CLK

The clock signal is an input that synchronizes the operation of the memory with other components in the system.

2. MEM_READ

The MEM_READ signal is an input that specifies whether the memory should read data from the specified address.

3. MEM_WRITE

The MEM_WRITE signal is an input that specifies whether the memory should write data to the specified address.

4. MEM_ADDRESS

The MEM_ADDRESS signal is an input that specifies the memory address to read from or write to.

5. funct3

funct3 is an input that is used to decode the instruction and determine the operation to be performed on the memory.

6. DATA_IN

The DATA_IN signal is an input that provides data to be written to the specified memory address.

Outputs


1. DATA_OUT

The DATA_OUT signal is an output that provides the data read from the specified memory address.

7. MUX 2 to 1

In the pipeline diagram, MUX1, MUX2, MUX3, PC MUX, MUXDATAMEM and MUXJAL are 2 to 1 MUXes. Each mux has two 32-bit inputs and a 32-bit output. Delay is not added to mux. The delay is not added to the MUX because the impact of adding delay to the MUX may depend on other components in the system. For example, if other components in the system already introduce significant delays, adding delays to the MUX may not have a significant impact on the overall performance.

Testbench of the MUX 2 to 1,

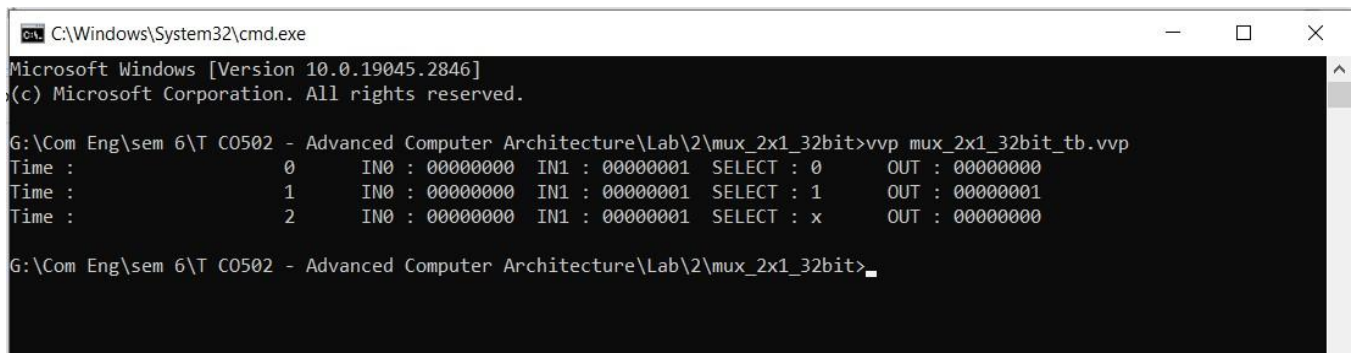

```
C:\Windows\System32\cmd.exe
Microsoft Windows [Version 10.0.19045.2846]
(c) Microsoft Corporation. All rights reserved.

G:\Com Eng\sem 6\T C0502 - Advanced Computer Architecture\Lab\2\mux_2x1_32bit>vvp mux_2x1_32bit_tb.vvp
Time :      0      IN0 : 00000000 IN1 : 00000001 SELECT : 0      OUT : 00000000
Time :      1      IN0 : 00000000 IN1 : 00000001 SELECT : 1      OUT : 00000001
Time :      2      IN0 : 00000000 IN1 : 00000001 SELECT : x      OUT : 00000000

G:\Com Eng\sem 6\T C0502 - Advanced Computer Architecture\Lab\2\mux_2x1_32bit>
```

8. MUX 5 to 1

Our design needs a 5 to 1 MUX to select the output of the SIGN/ZERO EXTEND unit. Our design can control five types of instructions, which are U type, I type, J type, S type, and B type. According to the MUXIMM_TYPE_SELECT signal, MUX selects one output. All inputs are 32-bit and all output is 32-bit.

The delay is not added to the MUX because the impact of adding delay to the MUX may depend on other components in the system. For example, if other components in the system already

introduce significant delays, adding delays to the MUX may not have a significant impact on the overall performance.

Testbench of the MUX 5 to 1,

```
Microsoft Windows [Version 10.0.19045.2846]
(c) Microsoft Corporation. All rights reserved.

G:\Com Eng\sem 6\T C0502 - Advanced Computer Architecture\Lab\2\mux_5x1_32bit>vvp mux_5x1_32bit_tb.vvp
Time :      0      IN0 : 00000000 IN1 : 00000001 IN2 : 00000010 IN3 : 00000011 IN4 : 00000100 SELECT : 000 OUT : 00000000
Time :      1      IN0 : 00000000 IN1 : 00000001 IN2 : 00000010 IN3 : 00000011 IN4 : 00000100 SELECT : 001 OUT : 00000001
Time :      2      IN0 : 00000000 IN1 : 00000001 IN2 : 00000010 IN3 : 00000011 IN4 : 00000100 SELECT : 010 OUT : 00000010
Time :      3      IN0 : 00000000 IN1 : 00000001 IN2 : 00000010 IN3 : 00000011 IN4 : 00000100 SELECT : 011 OUT : 00000011
Time :      4      IN0 : 00000000 IN1 : 00000001 IN2 : 00000010 IN3 : 00000011 IN4 : 00000100 SELECT : 100 OUT : 00000100
Time :      5      IN0 : 00000000 IN1 : 00000001 IN2 : 00000010 IN3 : 00000011 IN4 : 00000100 SELECT : xxx OUT : 00000000

G:\Com Eng\sem 6\T C0502 - Advanced Computer Architecture\Lab\2\mux_5x1_32bit>
```

9. 32-bit ADDER with PLUS 4

In the 32-bit adder, add an offset value to the PC in order to fetch the instruction at the correct address. The offset value is 4. PC is a register that holds the address of the next instruction to be fetched.

One input is the PC value, the other is 4, and the output is PC+4. Adder has a 1-unit delay. The reason is that the adder does computational work.

 


Figure 14: Adder with plus 4

Testbench of the adder,

```
G:\Com Eng\sem 6\T C0502 - Advanced Computer Architecture\Lab\2\adder_32bit_plus4>vvp adder_32bit_plus_4_tb.vvp
IN1 :      10      OUT :      14
IN1 :     128      OUT :     132

G:\Com Eng\sem 6\T C0502 - Advanced Computer Architecture\Lab\2\adder_32bit_plus4>
```

****Reason to skip implementation of FENCE AND FENCE.I instructions**

fence instructions are an important feature of the RISC-V architecture that provide memory ordering guarantees in multi-threaded programs and ensure correct execution of memory operations.

Here we are only implementing a single pipelined CPU. Therefore this CPU couldn't support multithreading. Because of that we didn't implement support for FENCE instructions in our CPU.